

SINGLE PHASE CONTROLLED RECTIFIERS

INTRODUCTION

- *Diodes of rectifier circuits in chp5 are replaced by thyristors.*
- *In thyristor based rectifiers, output voltage can be controlled. So they are termed as **controlled rectifiers**.*
- *Controlled rectifiers produce variable DC output, whose magnitude is varied by Phase control.*

Phase Control

DC output from rectifier is controlled by controlling duration of the conduction period by varying the point at which gate signal is applied to SCR.

- *Main drawback of phase control is Radio Frequency Interference (RFI)*

- Controlled rectifiers are of two types,

1- Fully Controlled rectifiers

DC current is unidirectional, but DC voltage has either polarity. With one polarity, flow of power is from AC source to DC load---Rectification.


With the reversal of DC voltage by the load, flow of power is from DC load to AC source---Inversion.

2- Half controlled rectifiers

Half of SCRs are replaced by diodes.


DC output current and voltage are unidirectional. i.e., flow of power is from AC source to DC load.

HALF-WAVE CONTROLLED RECTIFIERS

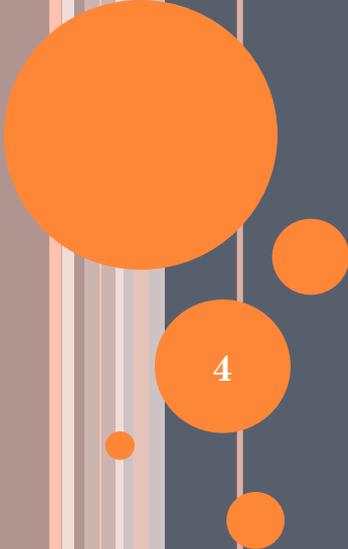


4

With Resistive Load


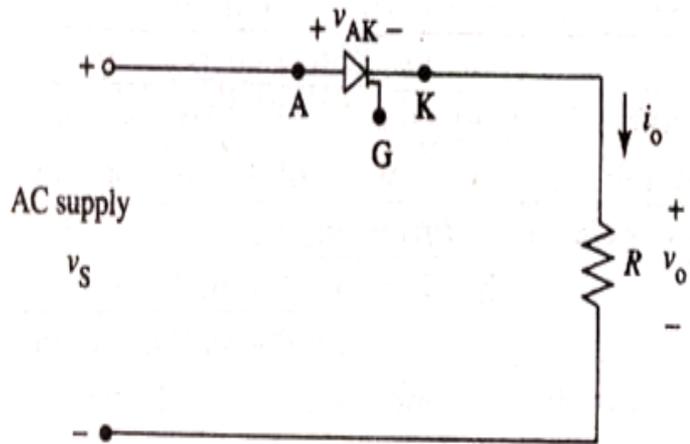


(a)


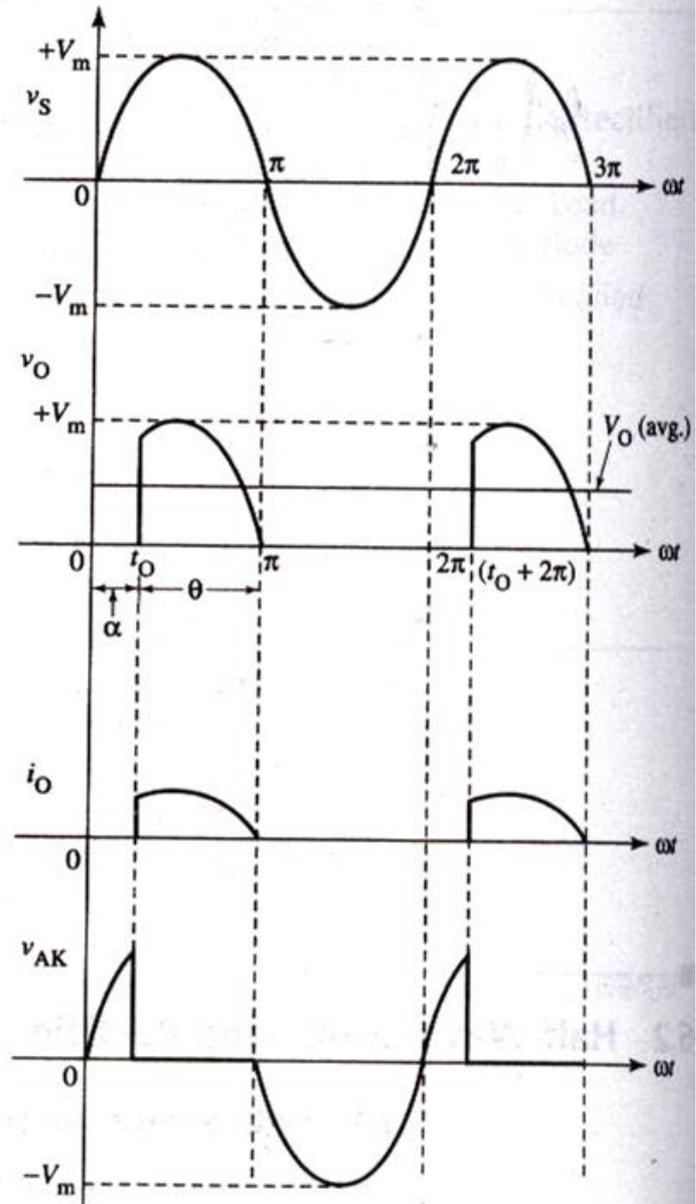


(b)


With an Inductive (RL) Load

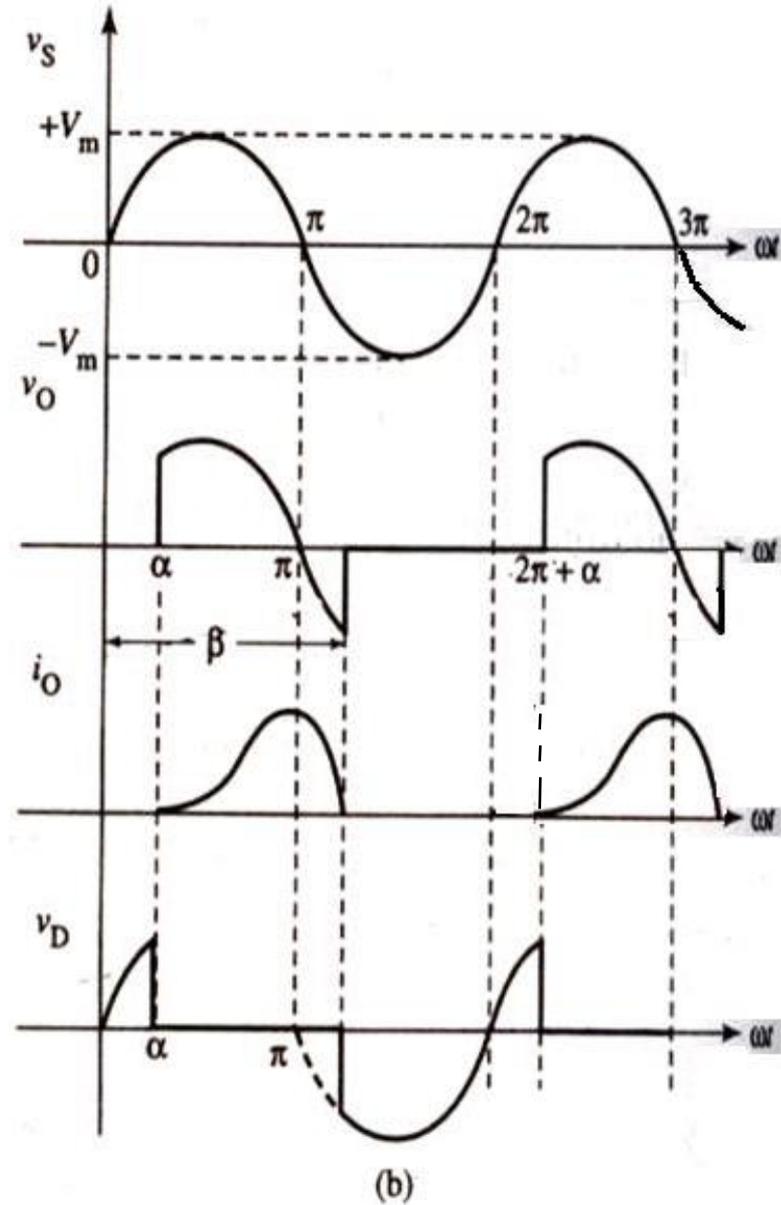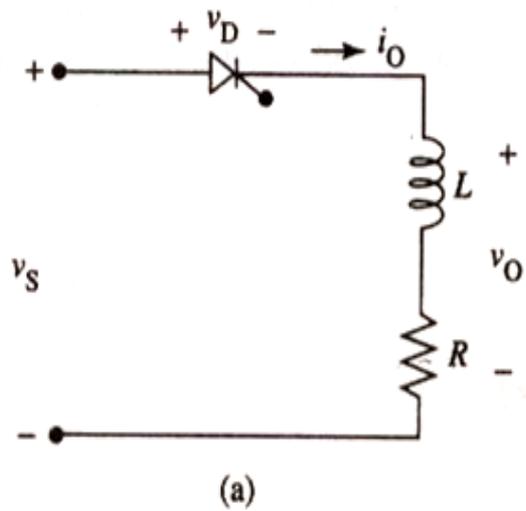

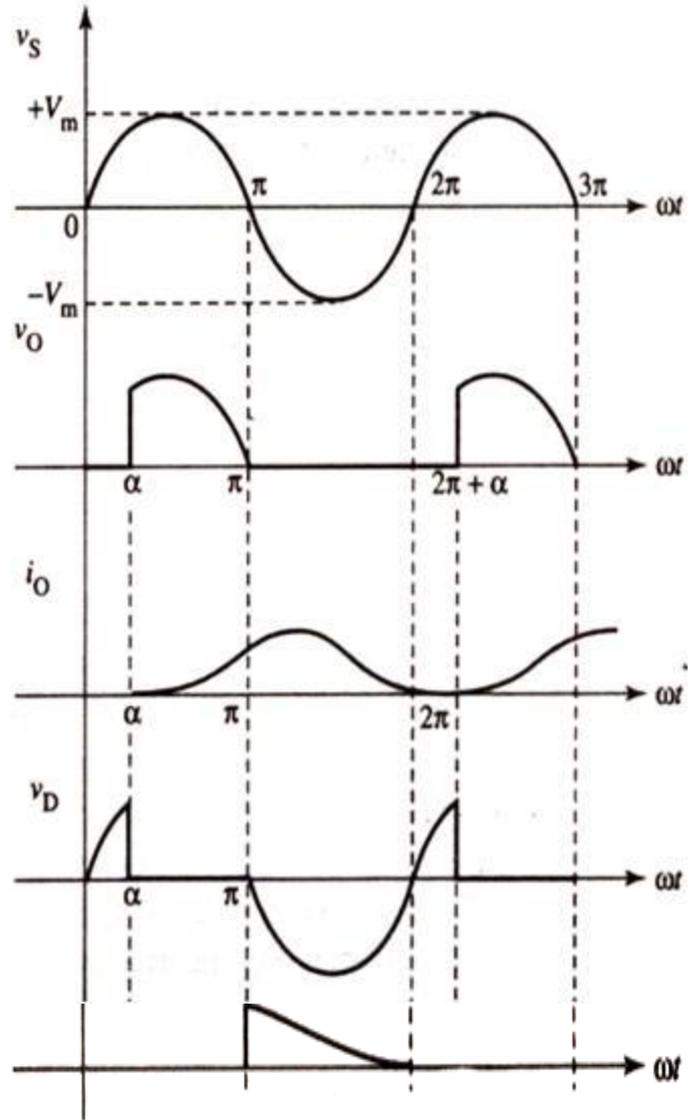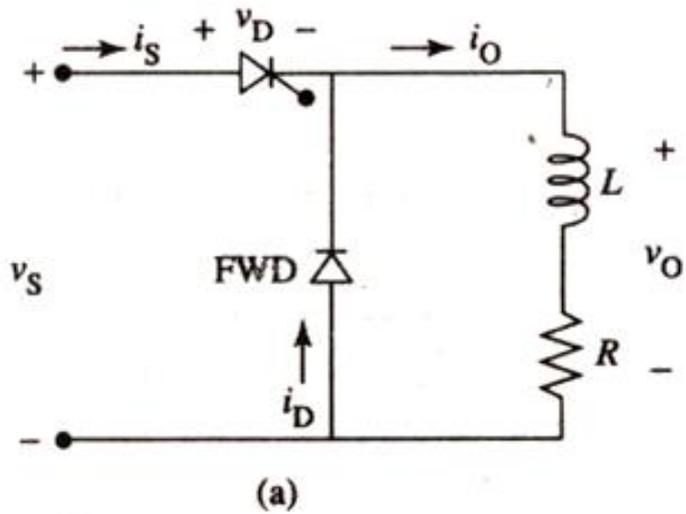With Inductive Load and Freewheeling Diode





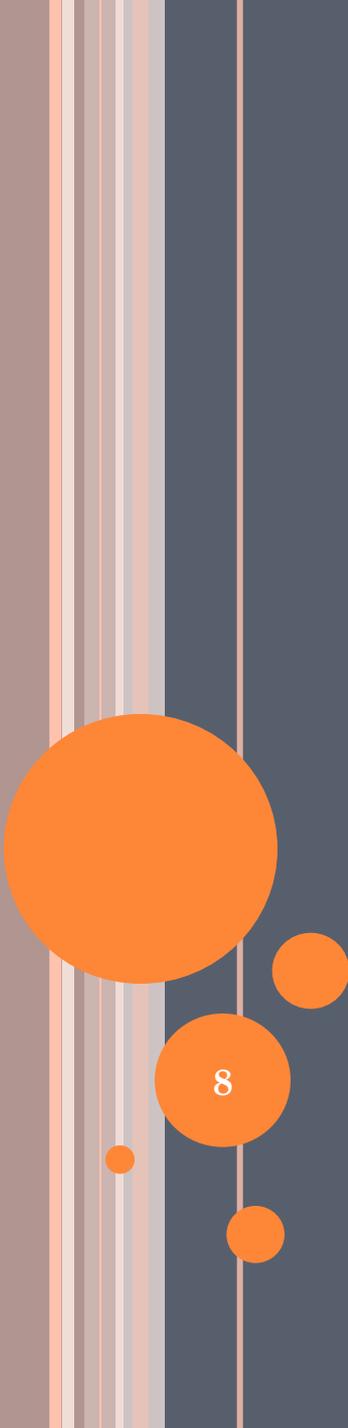FULL-WAVE CONTROLLED CENTER- TAP RECTIFIERS




8



With Resistive Load

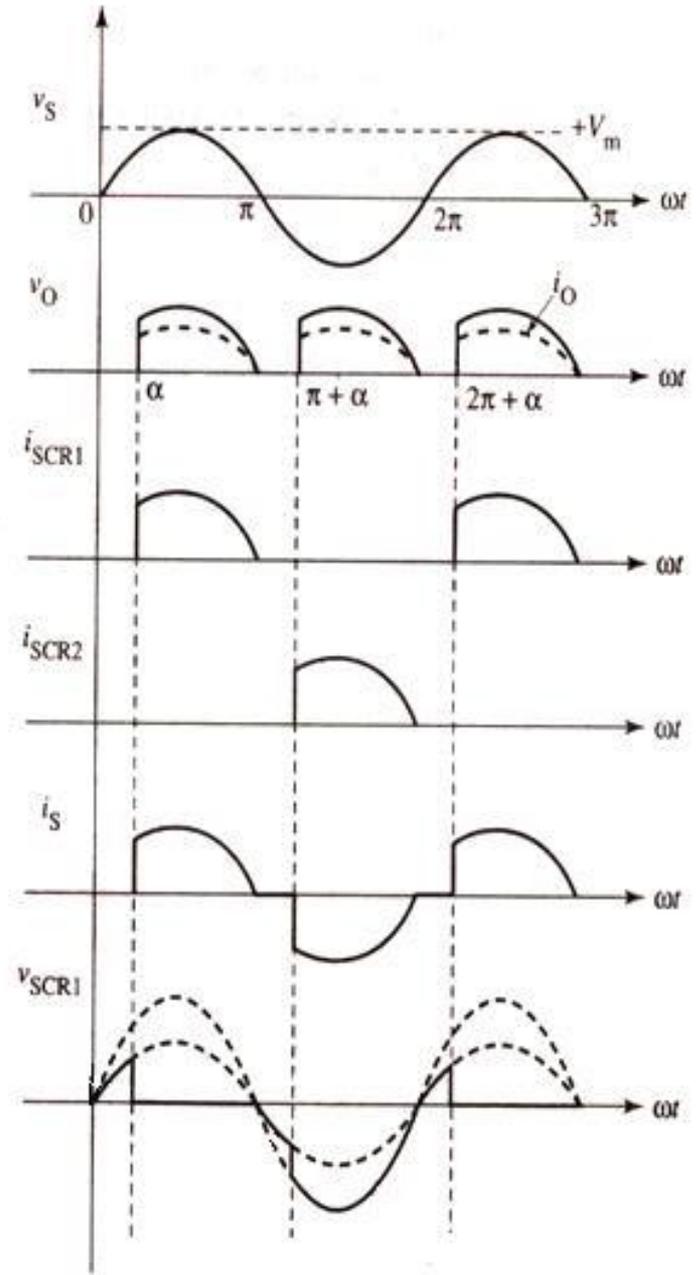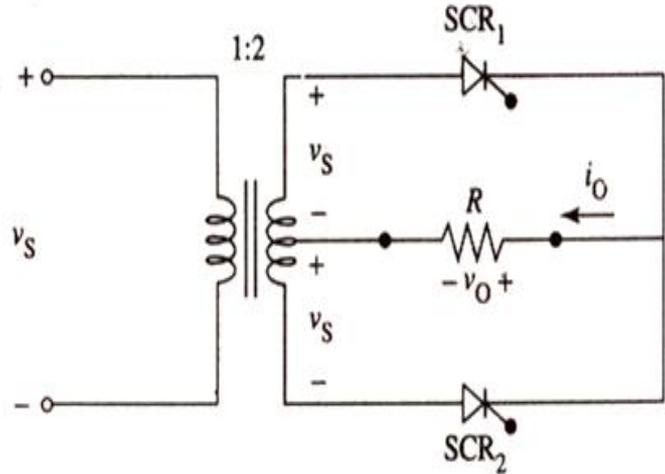

With an Inductive (RL) Load

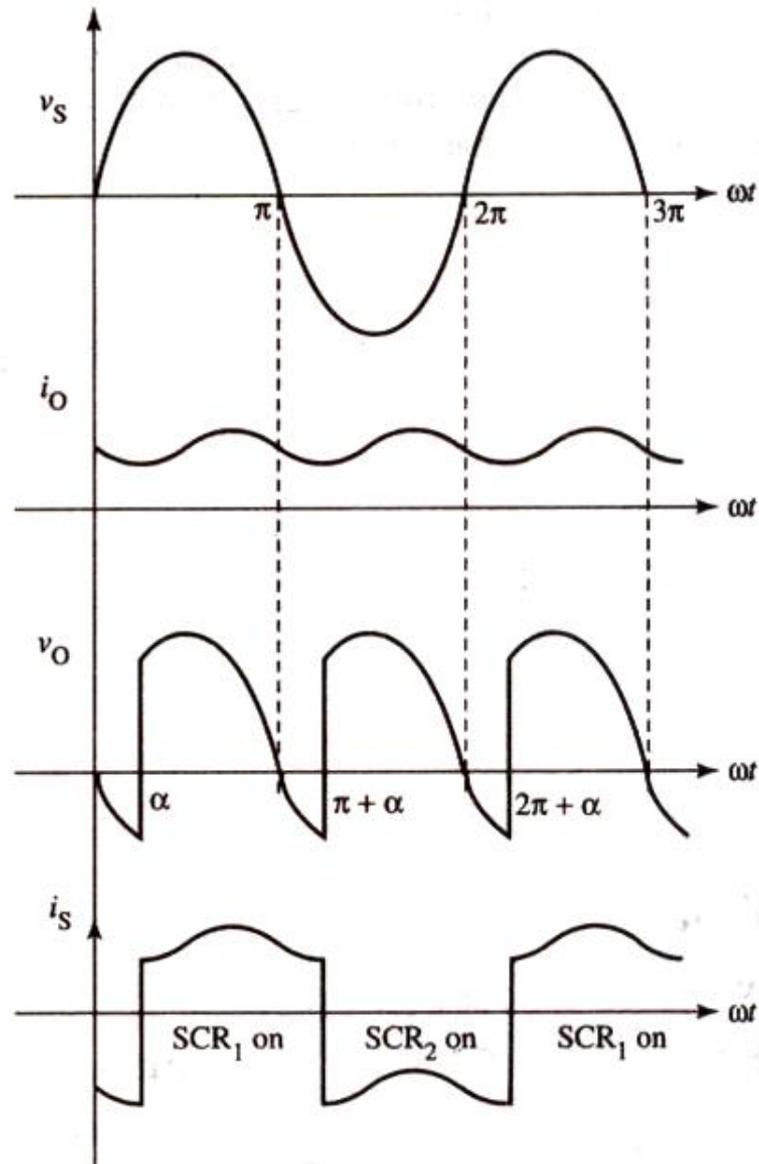

With Freewheeling Diode

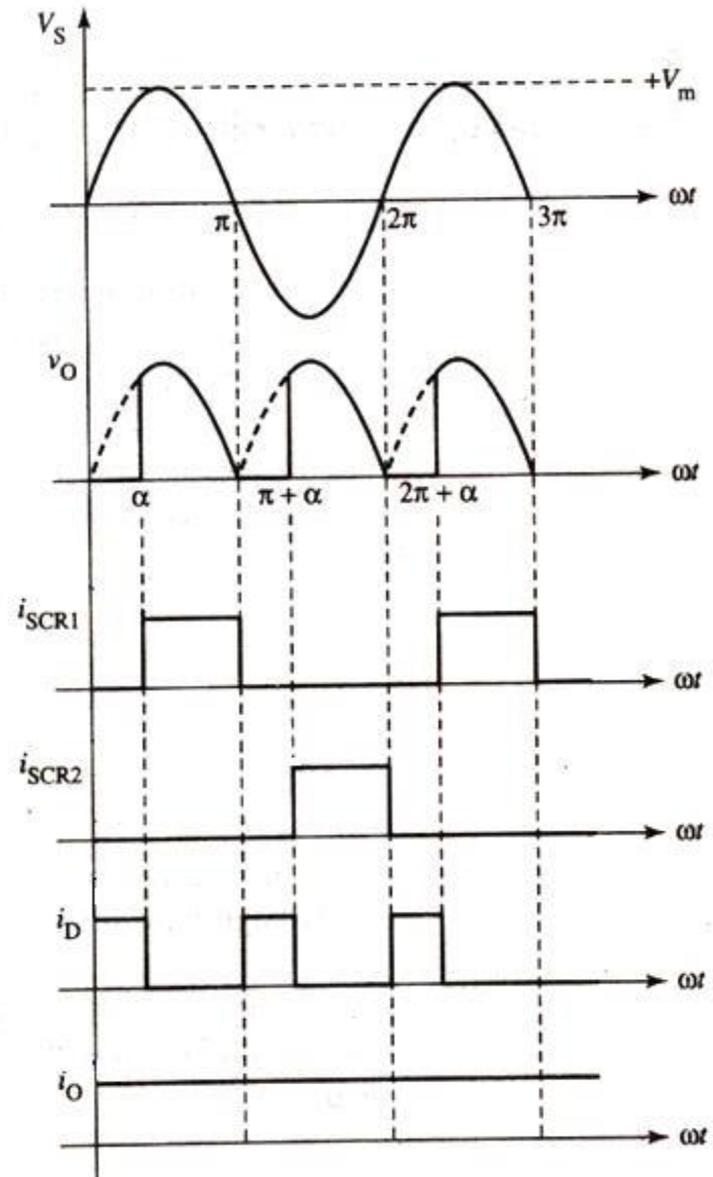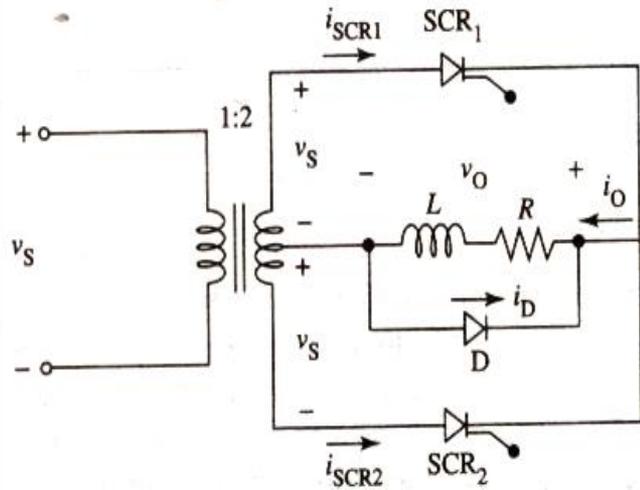

EXAMPLE 6.4


Explain with the help of waveforms the operation of a full-wave center-tap rectifier with RL load for the following firing angles:

- (a) 0°
- (b) 45°
- (c) 90°
- (d) 135°
- (e) 180°

Assume *highly Inductive* Load


Voltage and current waveforms for $\alpha=0^\circ$

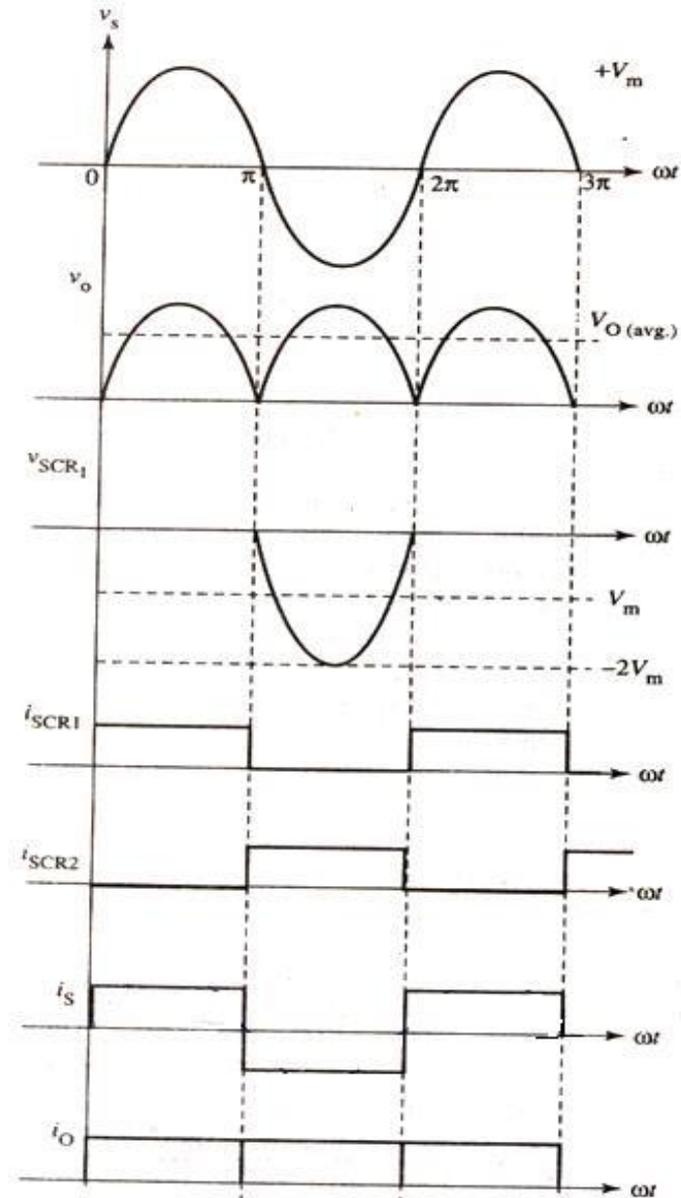- During positive-half cycle of source voltage, SCR1 is forward biased and SCR2 is reverse biased. During negative half-cycle, SCR2 is forward biased and SCR1 is reverse biased. In either case voltage across the load is V_s .
- Output is similar to uncontrolled rectifier.
- Each SCR conducts for 180° and supplies current to the load for this period




Voltage and current waveforms for $\alpha=45^\circ$

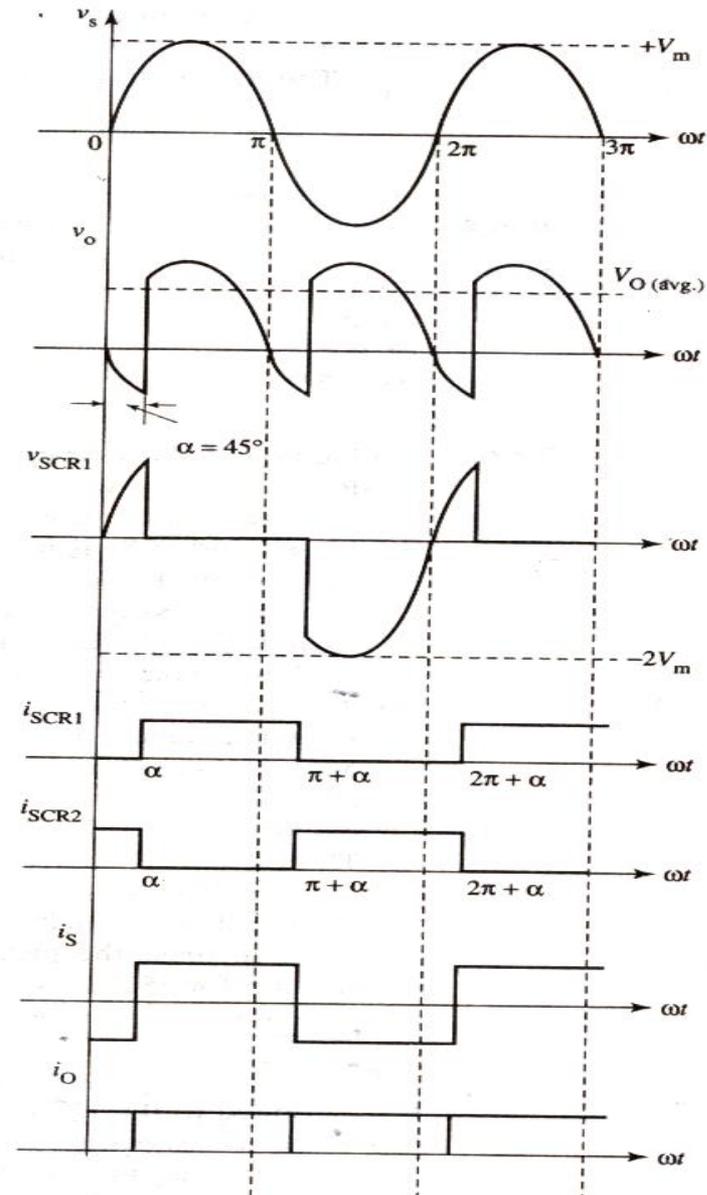- Average DC output voltage decreases.
- If SCR1 is triggered at 45° , SCR2 will conduct upto that point, even though the source voltage is zero, due to highly inductive nature of load.
- When SCR1 is turned on, SCR2 is turned off.
- Current to the load is supplied by SCR1 and SCR2, each conducting for 180°




Voltage and current waveforms for $\alpha=90^\circ$

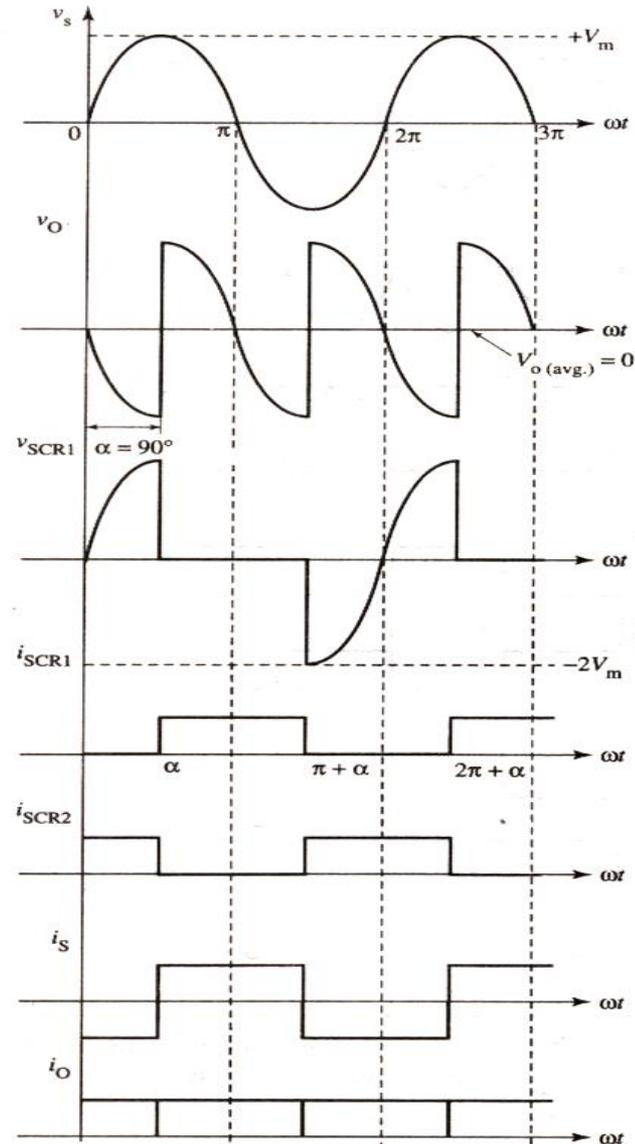- Average DC voltage is zero, so there is no transfer of power from AC source to DC load.
- Each SCR remains in conduction for 180°
- As firing angle is increased from 0 to 90° , the power supplied to the DC load decreases, becoming zero at $\alpha=90^\circ$




Voltage and current waveforms for $\alpha=135^\circ$

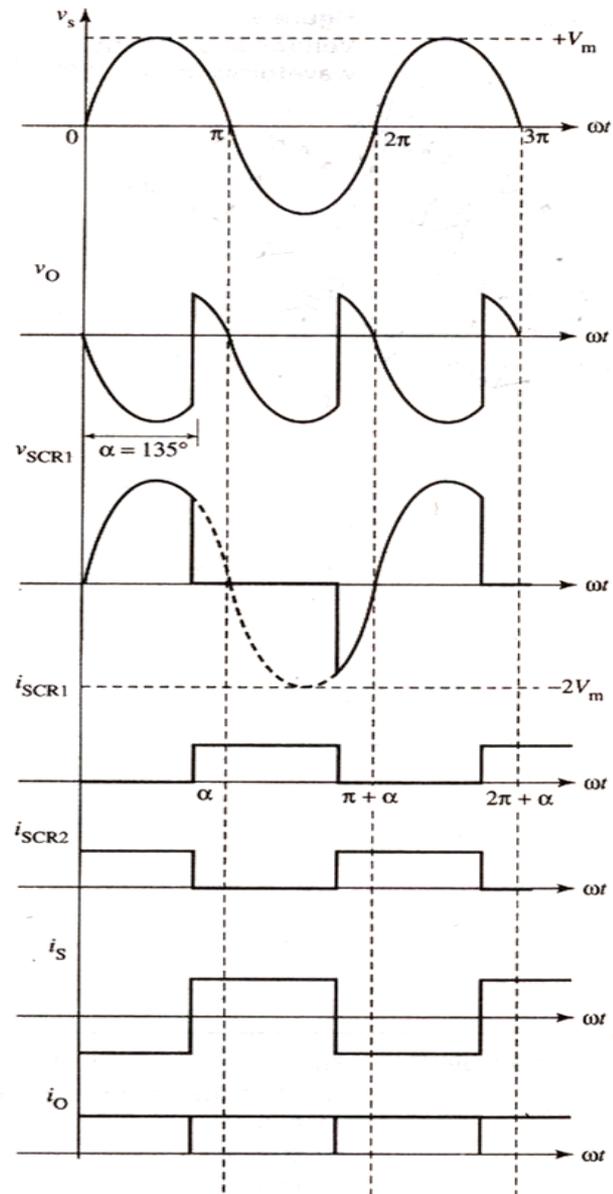- Average DC voltage is negative.
- Load current still flows in each SCR for 180° in its original direction.
- Load voltage has changed polarity.
- Power now flows from DC load to AC source .
- Circuit acts like an inverter.



Voltage and current waveforms for $\alpha=180^\circ$

- Average output DC voltage is at its maximum negative value.
- SCRs remain in conduction for 180°

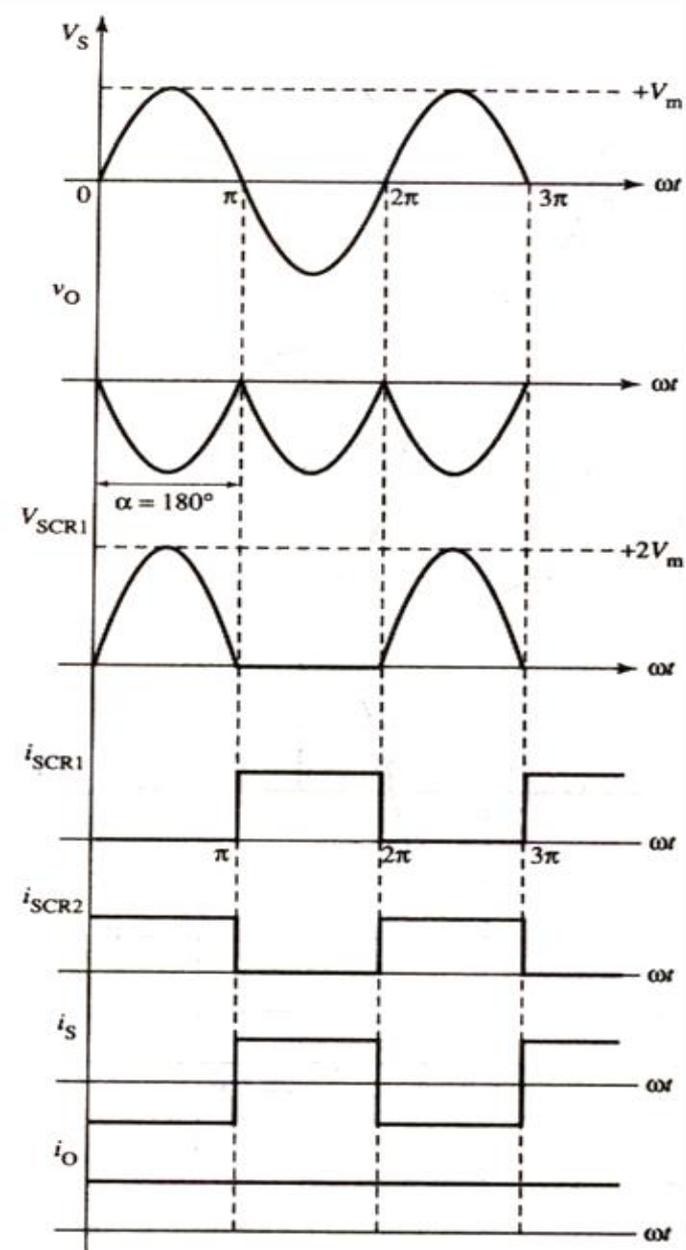

EXAMPLE 6.5

Show direction of power flow and operating mode (rectifying or inversion) of center-tap rectifier circuit with following firing angles:

- A) $\alpha > 0^\circ$
- B) $\alpha < 90^\circ$
- C) $\alpha > 90^\circ$
- D) $\alpha < 180^\circ$

SOLUTION


○ For firing angle in the range $0^\circ < \alpha < 90^\circ$

1. Average output voltage is positive.
2. Converter operates in the rectifying mode.
3. Power to the load is positive
4. Power flow is from AC source to the DC load.

○ For firing angle in the range $90^\circ < \alpha < 180^\circ$



1. Average output voltage is negative
2. Converter operates in inversion mode
3. Power to the load is negative
4. Power flow is from DC load to AC source

FULL-WAVE CONTROLLED BRIDGE RECTIFIER


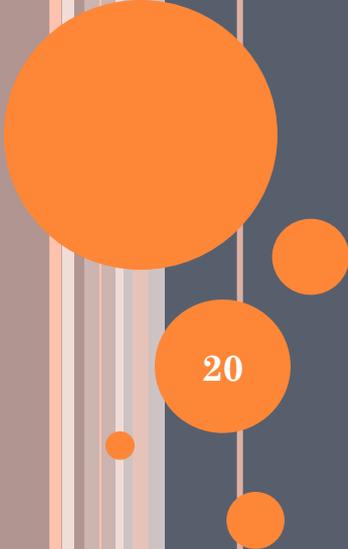


20


With Resistive Load

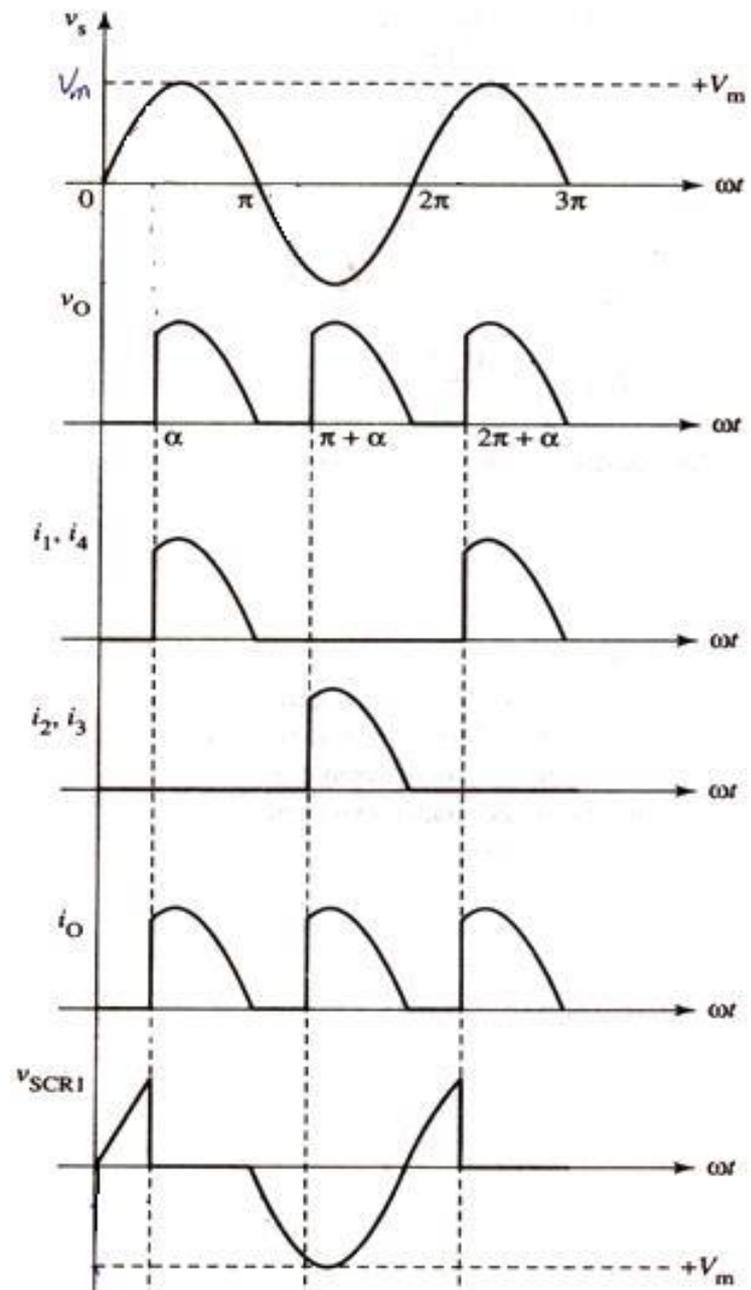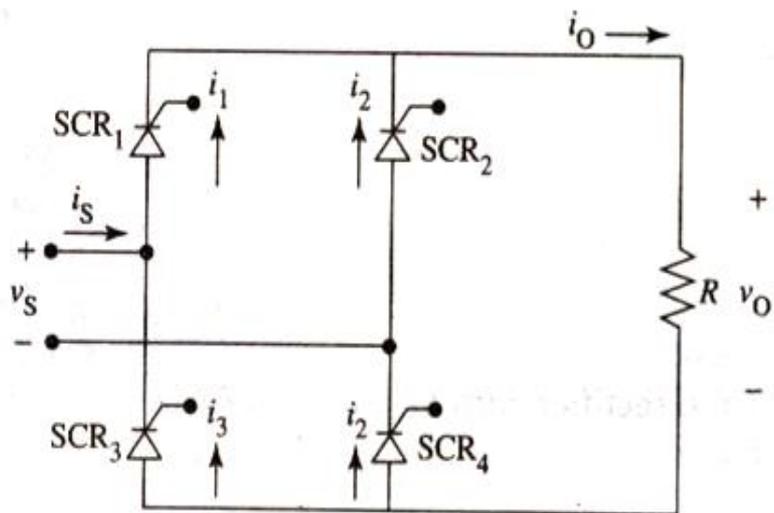



With an Inductive (RL) Load

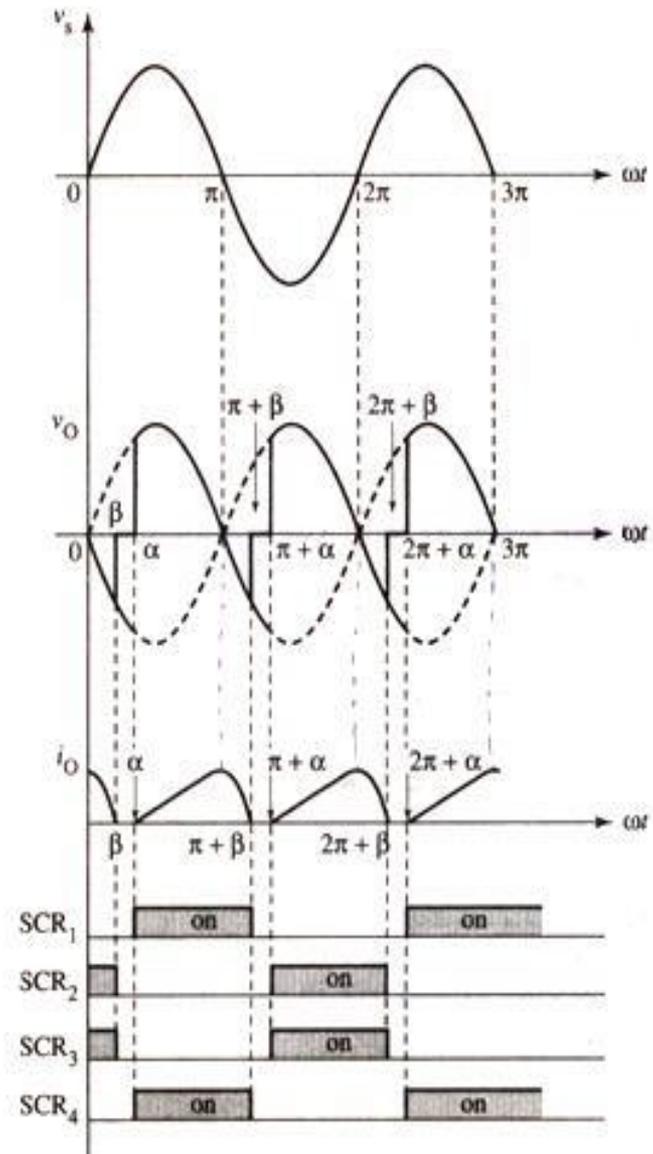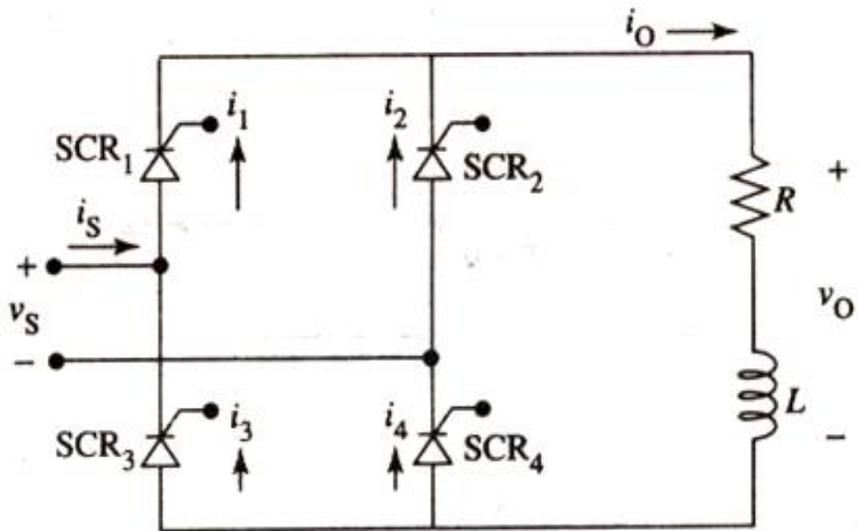

For $L \gg R$

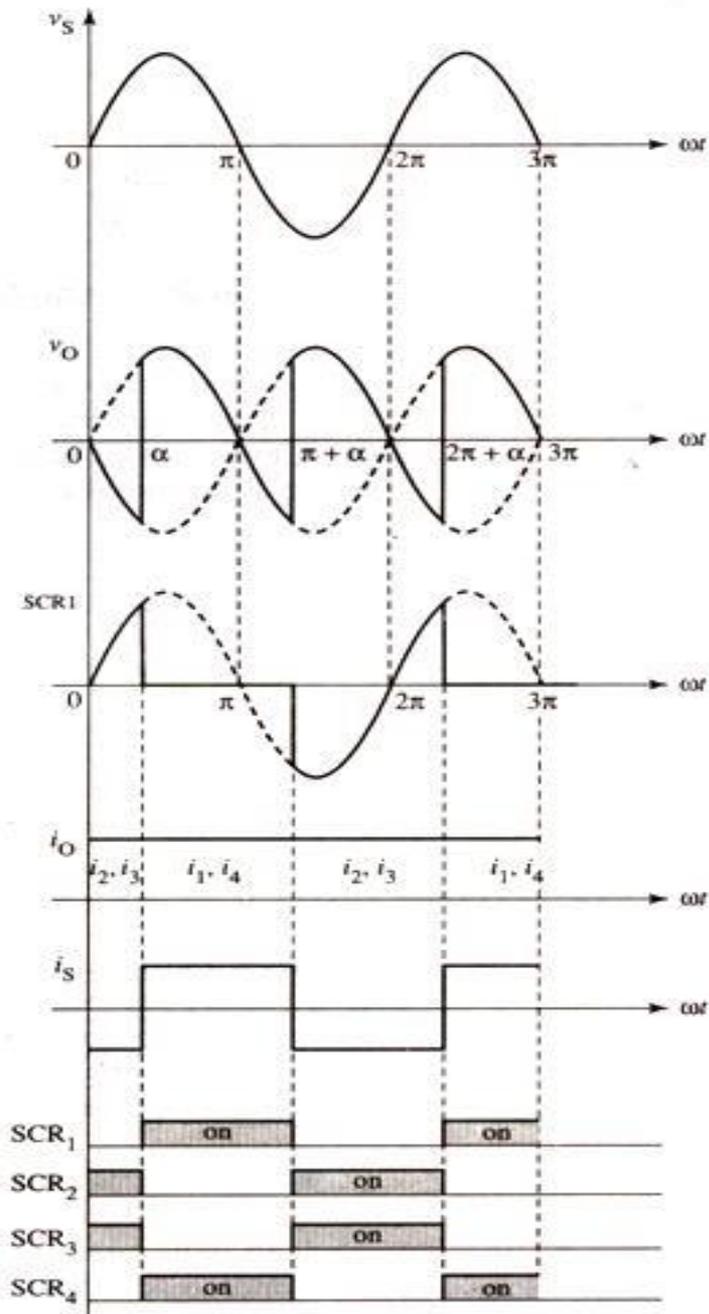



With RL load and freewheeling diode

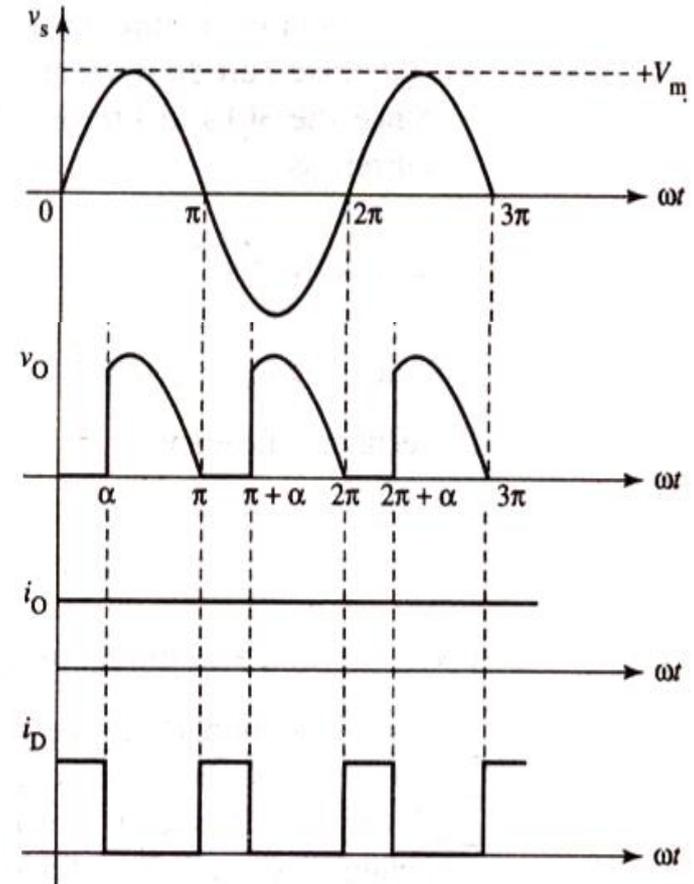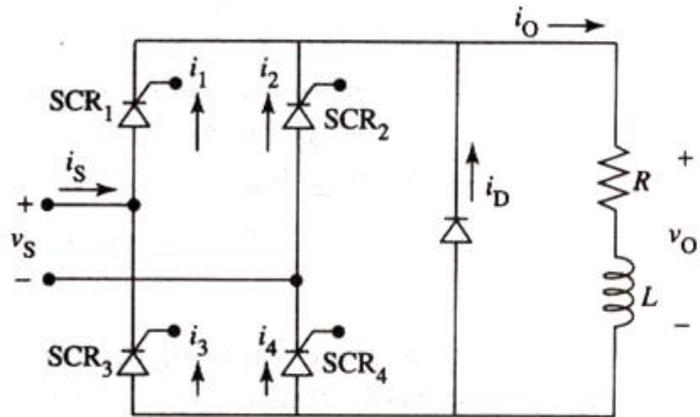

HALF-CONTROLLED OR SEMICONTROLLED BRIDGE RECTIFIERS

- In fully-controlled rectifier, only rectification can be obtained by connecting a freewheeling diode across the output terminals of the rectifier.
- Another method of obtaining rectification in bridge rectifiers is replacing half of the SCRs with diodes. These circuits are called semiconrolled bridge rectifiers.

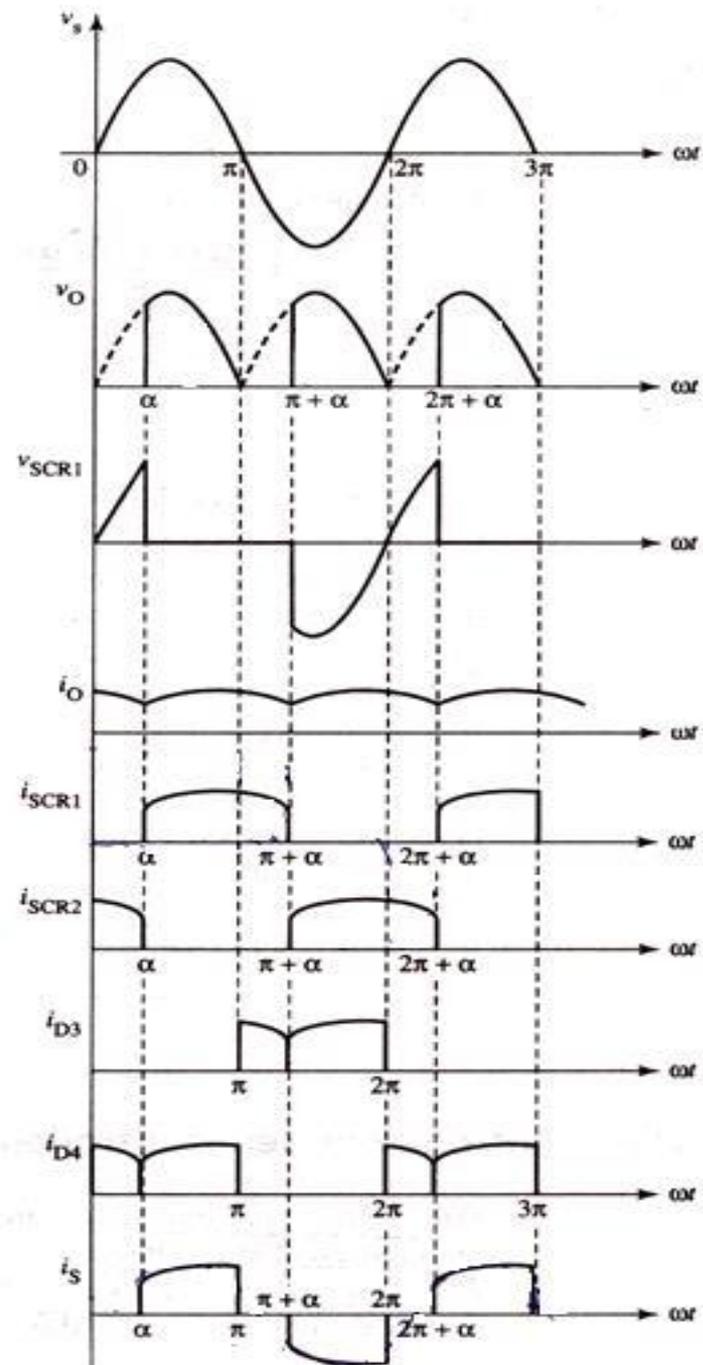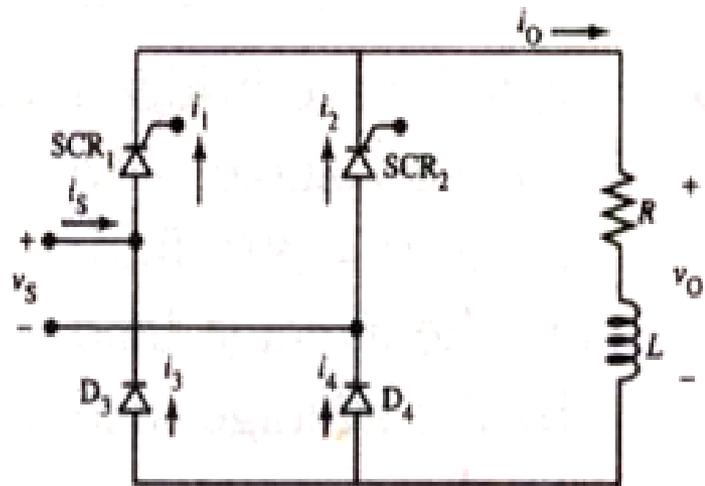Full-wave semicond controlled bridge rectifier circuit



Semiconrolled bridge rectifier with FWD

