

BJT Configuration

The current Amplification Factors

There are two current amplification factors in transistors.

1) α factor

2) β factor.

1) Current amplification factor α

It is the ratio of collector current (I_c) and Emitter current (I_E)

$$\alpha = \frac{I_c}{I_E}$$

value of $\alpha = 0.95$ to 0.99 .

→ For Common Base Configuration:

(i) For A.c signals

$$\alpha_{ac} = \frac{\Delta I_c}{\Delta I_E}$$

(ii) " D.c signals

$$\alpha_{dc} = \frac{I_c}{I_E}$$

2) Base current amplification factor β

It is the ratio of collector current I_c and base current I_B .

It is also called as transport factor in common emitter configuration.

1) For

A.c signals

$$\beta_{ac} = \frac{\Delta I_c}{\Delta I_B}$$

2)

D.c

"

$$\beta_{dc} = \frac{I_c}{I_B}$$

value of $\beta = 20$ to 100 .

Relation Between α and β

For transistor,
we know that

$$I_E = I_B + I_C \quad \text{--- (1)}$$

$$\text{eg } \beta = \frac{I_C}{I_B} \quad \text{--- (2)}$$

$$\alpha = \frac{I_C}{I_E} \quad \text{--- (3)}$$

Now, ' I_B ' divided by numerator & denominator

eg eq (3)

$$\alpha = \frac{I_C / I_B}{I_E / I_B}$$

$$\alpha = \frac{I_C / I_B}{I_E / I_B}$$

$$\therefore I_E = I_C + I_B$$

$$= \frac{I_C / I_B}{(I_C + I_B) / I_B} = \frac{I_C / I_B}{\frac{I_C}{I_B} + 1}$$

$$\boxed{\alpha = \frac{\beta}{1 + \beta}}$$

$$\therefore \beta = I_C / I_B$$

In term of α

$$\alpha(1 + \beta) = \beta$$

$$\alpha + \alpha\beta = \beta$$

$$\alpha = \beta - \alpha\beta$$

$$\alpha = \beta(1 - \alpha)$$

$$\frac{\alpha}{1 - \alpha} = \beta$$

So

$$\boxed{\beta = \frac{\alpha}{1 - \alpha}}$$